

Performance-based assessments for DC circuit competencies

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

The purpose of these assessments is for instructors to accurately measure the learning of their electronics students, in a way that melds theoretical knowledge with hands-on application. In each assessment, students are asked to predict the behavior of a circuit from a schematic diagram and component values, then they build that circuit and measure its real behavior. If the behavior matches the predictions, the student then simulates the circuit on computer and presents the three sets of values to the instructor. If not, then the student then must correct the error(s) and once again compare measurements to predictions. Grades are based on the number of attempts required before all predictions match their respective measurements.

You will notice that no component values are given in this worksheet. The *instructor* chooses component values suitable for the students' parts collections, and ideally chooses different values for each student so that no two students are analyzing and building the exact same circuit. These component values may be hand-written on the assessment sheet, printed on a separate page, or incorporated into the document by editing the graphic image.

This is the procedure I envision for managing such assessments:


1. The instructor hands out individualized assessment sheets to each student.
2. Each student predicts their circuit's behavior at their desks using pencil, paper, and calculator (if appropriate).
3. Each student builds their circuit at their desk, under such conditions that it is impossible for them to verify their predictions using test equipment. Usually this will mean the use of a multimeter only (for measuring component values), but in some cases even the use of a multimeter would not be appropriate.
4. When ready, each student brings their predictions and completed circuit up to the instructor's desk, where any necessary test equipment is already set up to operate and test the circuit. There, the student sets up their circuit and takes measurements to compare with predictions.
5. If any measurement fails to match its corresponding prediction, the student goes back to their own desk with their circuit and their predictions in hand. There, the student tries to figure out where the error is and how to correct it.
6. Students repeat these steps as many times as necessary to achieve correlation between all predictions and measurements. The instructor's task is to count the number of attempts necessary to achieve this, which will become the basis for a percentage grade.
7. (OPTIONAL) As a final verification, each student simulates the same circuit on computer, using circuit simulation software (Spice, Multisim, etc.) and presenting the results to the instructor as a final pass/fail check.

These assessments more closely mimic real-world work conditions than traditional written exams:

- Students cannot pass such assessments only knowing circuit theory or only having hands-on construction and testing skills – they must be proficient at both.
- Students do not receive the “authoritative answers” from the instructor. Rather, they learn to validate their answers through real circuit measurements.
- Just as on the job, the work isn't complete until *all errors* are corrected.
- Students must recognize and correct their own errors, rather than having someone else do it for them.
- Students must be fully prepared on exam days, bringing not only their calculator and notes, but also their tools, breadboard, and circuit components.

Instructors may elect to reveal the assessments before test day, and even use them as preparatory labwork and/or discussion questions. Remember that there is absolutely nothing wrong with “teaching to

the test” *so long as the test is valid*. Normally, it is bad to reveal test material in detail prior to test day, lest students merely memorize responses in advance. With performance-based assessments, however, there is no way to pass without truly understanding the subject(s).

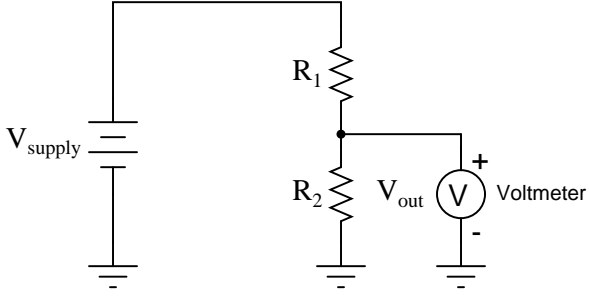Competency: Voltage divider circuit		Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 20px;">  </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> $V_{\text{supply}} =$ $V_{\text{out}} =$ </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>I_{supply}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td>I_{R1}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>V_{R1}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td>I_{R2}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>V_{R2}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> <div style="margin-top: 20px; display: flex; align-items: center;"> <div style="text-align: center; margin-right: 20px;"> $\frac{V_{\text{out}}}{V_{\text{supply}}}$ (Ratio) </div> <div style="display: flex; gap: 20px;"> <div style="text-align: center;"> Predicted <input style="width: 80px; height: 25px;" type="text"/> </div> <div style="text-align: center;"> Calculated (from measurements) <input style="width: 80px; height: 25px;" type="text"/> </div> </div> </div>				Predicted	Measured		Predicted	Measured	I_{supply}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>			
	Predicted	Measured		Predicted	Measured																					
I_{supply}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																					
V_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																					
V_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component <input style="width: 50px; height: 25px;" type="text"/> fails <input style="width: 30px; height: 20px;" type="checkbox"/> open <input style="width: 30px; height: 20px;" type="checkbox"/> other _____</p> <p><input style="width: 30px; height: 20px;" type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> </div>																										

file 03176

Answer 1

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 1

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Students will have to choose resistor values appropriate to the task.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Current divider circuit		Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> $I_{\text{supply}} =$ $I_{\text{out}} =$ </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>V_{supply}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td>V_{R1}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>I_{R1}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td>V_{R2}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>I_{R2}</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> <div style="margin-top: 20px; display: flex; align-items: center;"> <div style="text-align: center; margin-right: 10px;"> $\frac{I_{\text{out}}}{I_{\text{supply}}}$ (Ratio) </div> <div style="display: flex; justify-content: space-around; width: 100%;"> <div style="text-align: center;"> Predicted <input style="width: 80px; height: 25px;" type="text"/> </div> <div style="text-align: center;"> Calculated (from measurements) <input style="width: 80px; height: 25px;" type="text"/> </div> </div> </div>				Predicted	Measured		Predicted	Measured	V_{supply}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	I_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>			
	Predicted	Measured		Predicted	Measured																					
V_{supply}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																					
I_{R1}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	V_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																					
I_{R2}	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component <input style="width: 40px; height: 20px;" type="text"/> fails <input style="width: 20px; height: 15px;" type="checkbox"/> open <input style="width: 20px; height: 15px;" type="checkbox"/> other _____</p> <p><input style="width: 20px; height: 15px;" type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> <div style="height: 100px; border: 1px solid black; margin-top: 10px;"></div> </div>																										

file 03177

Answer 2

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 2

Use a variable-current, regulated power supply to supply any amount of DC current below a few milliamps. Students will have to choose resistor values appropriate to the task. I recommend low-value resistors so as to keep the voltage drop (and power dissipation!) low.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: **Series-parallel DC resistor circuit**

Version: _____

Schematic

Given conditions

$V_{\text{supply}} =$
 $R_1 =$
 $R_2 =$
 $R_3 =$

Parameters

	Predicted	Measured		Predicted	Measured
I_{supply}	<input type="text"/>	<input type="text"/>	I_{R1}	<input type="text"/>	<input type="text"/>
V_{R1}	<input type="text"/>	<input type="text"/>	I_{R2}	<input type="text"/>	<input type="text"/>
V_{R2}	<input type="text"/>	<input type="text"/>	I_{R3}	<input type="text"/>	<input type="text"/>
V_{R3}	<input type="text"/>	<input type="text"/>			

Fault analysis

Suppose component fails

☐ open
 ☐ other _____

☐ shorted

What will happen in the circuit?

Answer 3

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 3

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Series-parallel DC resistor circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
I_{supply}			I_{R1}
V_{R1}			I_{R2}
V_{R2}			I_{R3}
V_{R3}			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>			
<i>What will happen in the circuit?</i>			

file 01631

Answer 4

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 4

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Series-parallel DC resistor circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
I_{supply}			I_{R1}
V_{R1}			I_{R2}
V_{R2}			I_{R3}
V_{R3}			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>			
<i>What will happen in the circuit?</i>			

file 01632


Answer 5

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 5

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

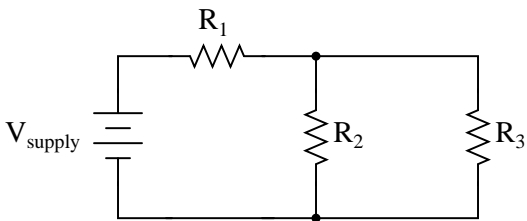Competency: Series-parallel DC resistor circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
I_{supply}			I_{R1}
V_{R1}			I_{R2}
V_{R2}			I_{R3}
V_{R3}			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>			
<i>What will happen in the circuit?</i>			

file 01630

Answer 6

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 6

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Series-parallel DC resistor circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_4 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
I_{supply}			I_{R1}
V_{R1}			I_{R2}
V_{R2}			I_{R3}
V_{R3}			I_{R4}
V_{R4}			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>			
<i>What will happen in the circuit?</i>			

Answer 7

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 7

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Series-parallel DC resistor circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_4 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
I_{supply}			I_{R1}
V_{R1}			I_{R2}
V_{R2}			I_{R3}
V_{R3}			I_{R4}
V_{R4}			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>			
<i>What will happen in the circuit?</i>			

Answer 8

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 8

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Series-parallel DC resistor circuit		Version:																																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> $V_{\text{supply}} =$ $R_1 =$ $R_2 =$ $R_3 =$ $R_4 =$ </div>																																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> <th style="width: 15%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>I_{supply}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{R1}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_{R1}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{R2}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_{R2}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{R3}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_{R3}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{R4}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_{R4}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>					Predicted	Measured		Predicted	Measured	I_{supply}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_{R1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_{R2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R3}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_{R3}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R4}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_{R4}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>			
	Predicted	Measured		Predicted	Measured																																		
I_{supply}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																																		
V_{R1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																																		
V_{R2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R3}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																																		
V_{R3}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{R4}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																																		
V_{R4}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component <div style="border: 1px solid black; width: 40px; height: 20px; display: inline-block;"></div> fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> </div>																																							

Answer 9

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 9

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Custom rheostat range		Version:																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;"> <pre> graph LR In(()) --- Node1(()) Node1 --- R1[R1] Node1 --- Rpot[Rpot] R1 --- Node2(()) Rpot --- Node2 Node2 --- R2[R2] R2 --- Out(()) </pre> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-between; margin-top: 10px;"> <div style="width: 45%;"> R_{total} (minimum) = </div> <div style="width: 45%;"> R_{total} (maximum) = </div> </div> <div style="margin-top: 10px;"> R_{pot} = </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Ideal</th> <th style="text-align: center;">Attained</th> <th></th> </tr> </thead> <tbody> <tr> <td style="width: 10%;">R_1</td> <td style="width: 20%;"><input style="width: 90%;" type="text"/></td> <td style="width: 20%;"><input style="width: 90%;" type="text"/></td> <td rowspan="2" style="width: 50%; vertical-align: middle; padding-left: 10px;"> Resistors R_1 and R_2 may need to be series-parallel networks in order to achieve the necessary values. </td> </tr> <tr> <td>R_2</td> <td><input style="width: 90%;" type="text"/></td> <td><input style="width: 90%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td style="text-align: center;">Measured</td> <td></td> </tr> <tr> <td>R_{total} (minimum)</td> <td></td> <td><input style="width: 90%;" type="text"/></td> <td></td> </tr> <tr> <td>R_{total} (maximum)</td> <td></td> <td><input style="width: 90%;" type="text"/></td> <td></td> </tr> </tbody> </table>				Ideal	Attained		R_1	<input style="width: 90%;" type="text"/>	<input style="width: 90%;" type="text"/>	Resistors R_1 and R_2 may need to be series-parallel networks in order to achieve the necessary values.	R_2	<input style="width: 90%;" type="text"/>	<input style="width: 90%;" type="text"/>			Measured		R_{total} (minimum)		<input style="width: 90%;" type="text"/>		R_{total} (maximum)		<input style="width: 90%;" type="text"/>	
	Ideal	Attained																							
R_1	<input style="width: 90%;" type="text"/>	<input style="width: 90%;" type="text"/>	Resistors R_1 and R_2 may need to be series-parallel networks in order to achieve the necessary values.																						
R_2	<input style="width: 90%;" type="text"/>	<input style="width: 90%;" type="text"/>																							
		Measured																							
R_{total} (minimum)		<input style="width: 90%;" type="text"/>																							
R_{total} (maximum)		<input style="width: 90%;" type="text"/>																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> Suppose component <input style="width: 50px;" type="text"/> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div> </div> <p style="margin-top: 10px;"><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>																									

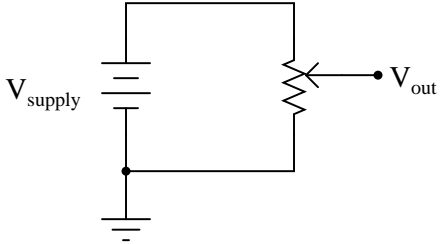
file 01754

Answer 10

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 10

Be sure to remind your students that resistances R_1 and R_2 may need to be series-parallel networks in themselves, to achieve the necessary values. An alternative you may wish to permit is the use of 10-turn (precision) potentiometers connected as rheostats for R_1 and R_2 . This way the circuit's minimum and maximum values may be precisely calibrated. The main potentiometer, R_{pot1} , should be a 3/4 turn unit, to allow fast checking of minimum and maximum total resistance, and it should be some common value such as 1 k Ω or 10 k Ω .

Competency: Potentiometer as voltage divider	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Description</div> <p style="margin-top: 10px;">You must set the potentiometer to the correct position to achieve V_{out} given V_{supply} <i>before</i> it is connected to V_{supply} for testing.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div>$V_{supply} =$</div> <div>$V_{out} =$</div> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="margin-top: 20px;"> <div style="display: flex; align-items: center; margin-bottom: 20px;"> <div style="margin-right: 10px;">V_{out}</div> <div style="text-align: center;"> <p>Measured</p> <input style="width: 100px; height: 25px;" type="text"/> </div> </div> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">Error (%)</div> <div style="text-align: center; flex-grow: 1;"> <p>Calculated</p> <input style="width: 100px; height: 25px;" type="text"/> </div> <div style="margin-left: 20px;"> $\frac{V_{out(actual)} - V_{out(ideal)}}{V_{out(ideal)}} \times 100\%$ </div> </div> </div>	

file 01925

Answer 11

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 11

Students need not measure potentiometer shaft angles in order to do this exercise. Rather, all they need to do is measure resistance between the wiper and the two outer terminals to set the potentiometer to a position where it will produce the specified division of voltage.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Kirchhoff's Voltage Law		Version:																																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;"> </div>																																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;">$V_{\text{supply}} = \text{Any whole-number value evenly divisible by 4}$</p> <p>$R_1 = R_2 = R_3 = R_4 =$</p>																																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="padding: 5px;">V_{R1}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="padding: 5px;">V_{R3}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="padding: 5px;">V_{R2}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="padding: 5px;">V_{R4}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="padding: 5px;">V_{BD}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="padding: 5px;">V_{DA}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="padding: 5px;">V_{BE}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="padding: 5px;">V_{DC}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="padding: 5px;">V_{AC}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="padding: 5px;">V_{CE}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> </tbody> </table> <p style="text-align: center; margin-top: 20px;"><i>Note: "V_{BD}" means voltage measured with the red lead touching B and the black lead touching D.</i></p>					Predicted	Measured		Predicted	Measured	V_{R1}			V_{R3}			V_{R2}			V_{R4}			V_{BD}			V_{DA}			V_{BE}			V_{DC}			V_{AC}			V_{CE}		
	Predicted	Measured		Predicted	Measured																																		
V_{R1}			V_{R3}																																				
V_{R2}			V_{R4}																																				
V_{BD}			V_{DA}																																				
V_{BE}			V_{DC}																																				
V_{AC}			V_{CE}																																				

file 03294

Answer 12

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 12

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Kirchhoff's Current Law	Version:																		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;"> </div>																			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;">$I_{\text{supply}} = \text{Any whole-number milliamp value evenly divisible by 4}$</p> <p>$R_1 = R_2 = R_3 = R_4 = R_5 =$</p>																			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>I_{R1}</td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> <td>I_{R3}</td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> </tr> <tr> <td>I_{R2}</td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> <td>I_{R4}</td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> </tr> </tbody> </table> <p style="margin-top: 20px; text-align: center;">Sketch directions and magnitudes of currents at these nodes:</p> <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 10px;"> <div style="text-align: center;"> <p>A</p> </div> <div style="text-align: center;"> <p>B</p> </div> <div style="text-align: center;"> <p>C</p> </div> <div style="text-align: center;"> <p>D</p> </div> </div>			Predicted	Measured		Predicted	Measured	I_{R1}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	I_{R3}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	I_{R2}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	I_{R4}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>
	Predicted	Measured		Predicted	Measured														
I_{R1}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	I_{R3}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>														
I_{R2}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	I_{R4}	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>														

file 03593

Answer 13

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 13

I recommend students use a normal regulated (voltage) power supply, adjusting the output voltage until the output current is at 4 mA. 1 k Ω resistors work well for this circuit, requiring only 6.4 volts from the power supply to achieve 4 mA total current.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Loaded voltage divider		Version:																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;"> $V_{\text{supply}} =$ $R_1 =$ $R_2 =$ $R_3 =$ $R_{\text{load1}} =$ $R_{\text{load2}} =$ </p>																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>I_{supply}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{load1}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_A</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{load2}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> <tr> <td>V_B</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td>I_{bleed}</td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td> </tr> </tbody> </table>					Predicted	Measured		Predicted	Measured	I_{supply}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{load1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_A	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{load2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	V_B	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{bleed}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>
	Predicted	Measured		Predicted	Measured																						
I_{supply}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{load1}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																						
V_A	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{load2}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																						
V_B	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	I_{bleed}	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>																						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p style="margin-top: 10px;"> Suppose component <div style="border: 1px solid black; width: 40px; height: 20px; display: inline-block;"></div> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div> </p> <p style="margin-top: 10px;"><i>What will happen in the circuit?</i></p> <div style="height: 100px; border: 1px solid black; margin-top: 10px;"></div>																											

file 01609

Answer 14

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 14

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k 47k, 68k, 82k, etc.).

I have used this circuit as both a "quick" lab exercise and a troubleshooting exercise, using values of 10 k Ω for R1, R2, and R3; 15 k Ω for R(load1); 22 k Ω for R(load2); and 6 volts for the power supply. Of course, these component values are not critical, but they do provide easy-to measure voltages and currents without incurring excessive impedances that would cause significant voltmeter loading problems.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Loaded voltage divider		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_{\text{load1}} =$	$R_{\text{load2}} =$	$R_{\text{load3}} =$	
Parameters			
Predicted	Measured	Predicted	Measured
I_{supply}		I_{load1}	
V_A		I_{load2}	
V_B		I_{load3}	
		I_{bleed}	
Fault analysis			
Suppose component fails		<input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted	
<i>What will happen in the circuit?</i>			

file 01642


Answer 15

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 15

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

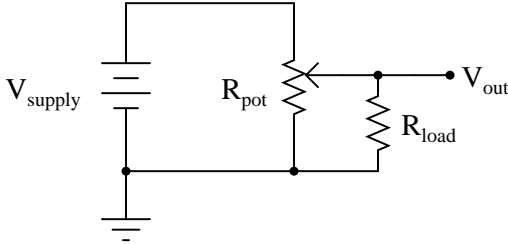Competency: Potentiometer as loaded voltage divider Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div> <p style="margin-top: 10px;">You must set the potentiometer to the correct position to achieve V_{out} given V_{supply} <i>before</i> it is connected to V_{supply} for testing.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div> <div style="margin-top: 20px;"> $V_{supply} =$ $V_{out} =$ $R_{pot} =$ $R_{load} =$ </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div> <div style="margin-top: 20px;"> <div style="text-align: center;">Measured</div> <div style="display: flex; align-items: center; margin-bottom: 20px;"> V_{out} <div style="border: 1px solid black; width: 100px; height: 30px; margin-left: 10px;"></div> </div> <div style="text-align: center;">Calculated</div> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">Error (%)</div> <div style="border: 1px solid black; width: 100px; height: 30px; margin-right: 10px;"></div> <div> $\frac{V_{out(actual)} - V_{out(ideal)}}{V_{out(ideal)}} \times 100\%$ </div> </div> </div>	

file 01926

Answer 16

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 16

Students need not measure potentiometer shaft angles in order to do this exercise. Rather, all they need to do is measure resistance between the wiper and the two outer terminals to set the potentiometer to a position where it will produce the specified division of voltage.

R_{pot} refers to the potentiometer's nominal full-range value (for example, 1 k Ω or 5 k Ω), and not to its particular setting. The setting is what the student must figure out to achieve V_{out} .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Wheatstone bridge		Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="margin-top: 10px;"> $V_{\text{supply}} =$ $R_1 =$ $R_2 =$ $R_3 =$ </div>											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>R_{pot} (balance)</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td>I_{supply}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </tbody> </table>				Predicted	Measured	R_{pot} (balance)			I_{supply}		
	Predicted	Measured									
R_{pot} (balance)											
I_{supply}											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p style="margin-left: 100px;"><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> <div style="border: 1px solid black; height: 150px; margin-top: 10px;"></div> </div>											

file 01618


Answer 17

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 17

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.), and be sure to specify a potentiometer value in excess of the amount required to balance the bridge.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

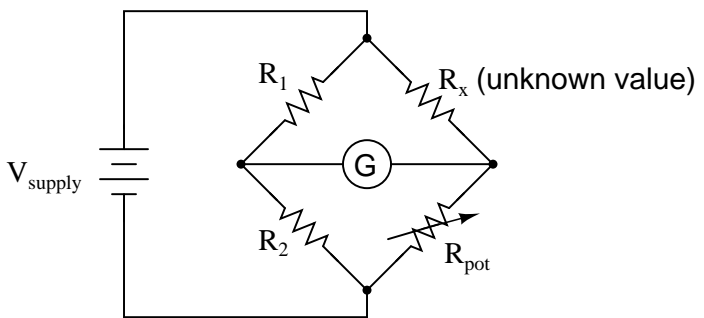Competency: Bridge resistance measurement		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$
$R_{\text{pot}} =$ Decade resistance box		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
R_x	Measured by bridge <div style="border: 1px solid black; width: 80px; height: 20px; margin: 0 auto;"></div>	Measured by ohmmeter <div style="border: 1px solid black; width: 80px; height: 20px; margin: 0 auto;"></div>
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Calculations</div>		

file 01643


Answer 18

The ohmmeter's indication is the "final word" on resistance.

Notes 18

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Use precision resistors for R_1 and R_2 , and use any standard resistor value for R_x between 1 k Ω and 100 k Ω .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

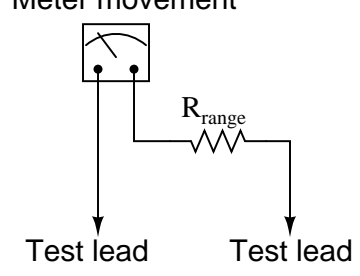Competency: DC voltmeter circuit	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> <p>Meter movement</p>  <p>Test lead Test lead</p> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="margin-top: 20px;"> $I_{F.S.} =$ $R_{\text{movement}} =$ Full-scale range = </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="margin-top: 20px;"> <div style="display: flex; justify-content: center; align-items: center; margin-bottom: 10px;"> <div style="margin-right: 10px;">R_{range}</div> <div style="text-align: center;"> <p>Predicted</p> <div style="border: 1px solid black; width: 100px; height: 25px;"></div> </div> </div> <div style="display: flex; justify-content: center; align-items: center;"> <div style="margin-right: 10px;">Meter indication with full-scale voltage applied</div> <div style="display: flex; gap: 10px;"> <div style="text-align: center;"> <p>Predicted</p> <div style="border: 1px solid black; width: 100px; height: 25px;"></div> </div> <div style="text-align: center;"> <p>Measured</p> <div style="border: 1px solid black; width: 100px; height: 25px;"></div> </div> </div> </div> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>	

file 01649


Answer 19

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 19

Students may use potentiometers in their range resistance networks to achieve precise values. However, they are not allowed to adjust those potentiometers after connecting them to the meter movement – they must set their potentiometer(s) during the "prediction" step of the assessment before the circuit is completely built.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

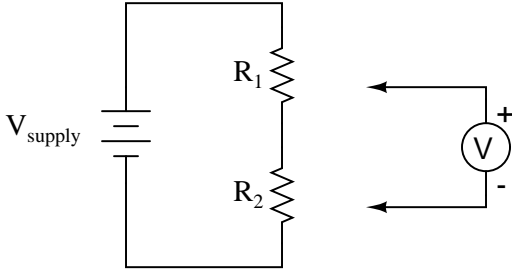Competency: Voltmeter loading	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="margin-top: 20px;"> $V_{\text{supply}} =$ $R_1 =$ $R_2 =$ </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Explanation</div> <div style="margin-top: 20px;"> <p>Due to the effects of the voltmeter "loading" the voltage divider circuit, there will be a significant difference between V_{R_2} predicted and V_{R_2} measured.</p> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="margin-top: 20px;"> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-bottom: 20px;"> <div style="text-align: right; padding-right: 10px;">V_{R_2}</div> <div style="text-align: center;"> <p>Predicted</p> <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div> </div> <div style="text-align: left; padding-left: 10px;">(Ideal, with no meter connected)</div> </div> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-bottom: 20px;"> <div style="text-align: right; padding-right: 10px;">V_{R_2}</div> <div style="text-align: center;"> <p>Measured</p> <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div> </div> <div style="text-align: left; padding-left: 10px;">(Real measurement with voltmeter)</div> </div> <div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: right; padding-right: 10px;">R_{input} (Meter)</div> <div style="text-align: center;"> <p>Calculated</p> <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div> </div> <div style="text-align: center;"> <p>Advertised</p> <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div> </div> </div> </div>	

file 01694

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 20

Be sure to specify resistor values for the voltage divider that will show a marked impact when measured with the type of voltmeter you expect your students to use. If you size the resistors for a modest impact measured with an analog voltmeter ($20,000 \Omega/\text{Volt}$), your students may not see much of an impact when using a modern digital voltmeter ($Z_{in} > 10 \text{ M}\Omega$).

New students often have a difficult time grasping the main idea of this activity, due to the assumption of the voltmeter's indication always being taken as true. The purpose of this activity is to shatter that assumption: to teach students that electrical measurements are never truly passive – rather, they invariably impact the circuit being measured in some way. Usually, the impact is so small it may be safely ignored. Here, due to the large resistor values used in the divider circuit, the impact of voltmeter usage on the circuit is non-trivial.

Another aspect of this activity that escapes some students' attention is that the circuit must be analyzed twice: once with the meter connected and once without. The point here is that the meter *becomes a component of the circuit when it is connected across R_2 , and thus changes all the voltages and currents.*

Competency: Self-induction	Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 20px;"> <p style="margin: 0;">Pushbutton switch</p> <p style="margin: 0;">V_{supply}</p> <p style="margin: 0;">L_1</p> <p style="margin: 0;">Neon lamp</p> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin: 10px 0;">$V_{\text{supply}} =$</p>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 35%;"></th> <th colspan="2" style="text-align: center; font-style: italic;">Yes/no answers only</th> </tr> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Tested</th> </tr> </thead> <tbody> <tr> <td>Lamp across L_1</td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>Lamp across switch</td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> <tr> <td>Lamp across battery</td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td><input style="width: 80px; height: 25px;" type="text"/></td> <td><input style="width: 80px; height: 25px;" type="text"/></td> </tr> </tbody> </table>			Yes/no answers only			Predicted	Tested	Lamp across L_1			Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	Lamp across switch			Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>	Lamp across battery			Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>
	Yes/no answers only																								
	Predicted	Tested																							
Lamp across L_1																									
Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																							
Lamp across switch																									
Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																							
Lamp across battery																									
Lamp flashes?	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>																							

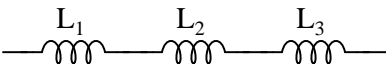
file 01646

Answer 21

The neon bulb will likely give you more reliable confirmation of your predictions than simulation software.

Notes 21

Students may either use ready-made inductors for this experiment (the larger the value, the more impressive the light flash!) or inductors of their own making (using old solenoid valve coils, or hand-wound coils around steel bolts). Power transformer primary windings also work well for this.

Competency: Series inductances		Version:
Schematic		
		
Given conditions		
$L_1 =$	$L_2 =$	$L_3 =$
Parameters		
L_{total}	Predicted <input style="width: 80px; height: 20px;" type="text"/>	Measured <input style="width: 80px; height: 20px;" type="text"/>
Analysis		
<div style="text-align: center;">Equation used to calculate L_{total} :</div>		

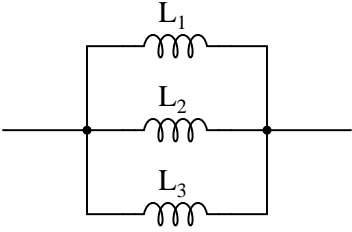
file 01650

Answer 22

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 22

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!

Competency: Parallel inductances		Version:
Schematic		
		
Given conditions		
$L_1 =$	$L_2 =$	$L_3 =$
Parameters		
L_{total}	Predicted <input style="width: 80px; height: 25px;" type="text"/>	Measured <input style="width: 80px; height: 25px;" type="text"/>
Analysis		
Equation used to calculate L_{total} :		

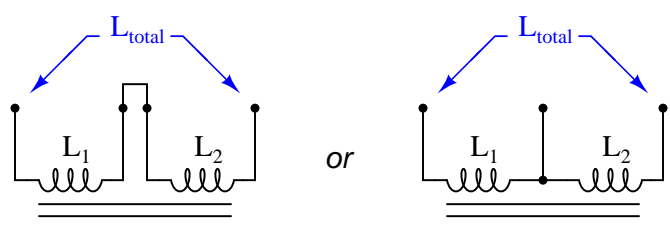
file 01651

Answer 23

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 23

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!

Competency: Series coupled inductors		Version:
Schematic		
		
Given conditions		
$L_1 =$ $L_2 =$		
Parameters		
L_{total}	Predicted <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div>	Measured <div style="border: 1px solid black; width: 100px; height: 30px; margin: 0 auto;"></div>
Analysis		
Equation used to calculate L_{total} :		


Answer 24

Use circuit simulation software to verify your predicted and measured parameter values.

You might be surprised to find that $L_{total} \neq L_1 + L_2$. This is due to the *mutual inductance* between inductors L_1 and L_2 .


Notes 24

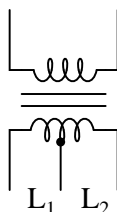In case students don't have access to a pair of inductors on a common core, they may either make their own by winding wire around a long ferromagnetic core, or use a center-tapped inductor (or transformer winding). The latter solution is probably the easiest:



Inexpensive audio output transformers (with center-tapped $1000\ \Omega$ primary windings) work very well for this. Your students' parts kits should contain at least one of these transformers anyway if they are to do audio coupling experiments later.

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!

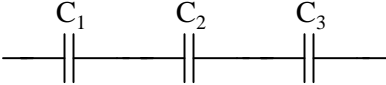Competency: Series capacitances		Version:
Schematic		
		
Given conditions		
$C_1 =$	$C_2 =$	$C_3 =$
Parameters		
C_{total}	Predicted <div style="border: 1px solid black; width: 100px; height: 25px; margin: 0 auto;"></div>	Measured <div style="border: 1px solid black; width: 100px; height: 25px; margin: 0 auto;"></div>
Analysis		
Equation used to calculate C_{total} :		

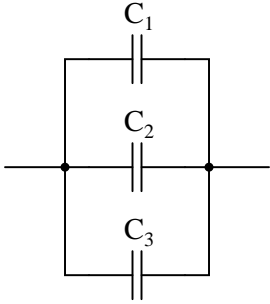
file 01652

Answer 25

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 25

Many modern digital multimeters come equipped with capacitance measurement built-in. If your students do not have these meters, you will either need to provide one for them to use, or provide an LCR meter. If you don't have either one of these instruments, you should get one right away!

Competency: Parallel capacitances		Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>								
								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>								
$C_1 =$ $C_2 =$ $C_3 =$								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>								
<table style="width: 100%; border-collapse: collapse;"><thead><tr><th style="width: 10%;"></th><th style="width: 20%; text-align: center;">Predicted</th><th style="width: 20%; text-align: center;">Measured</th></tr></thead><tbody><tr><td style="vertical-align: middle;">C_{total}</td><td style="text-align: center;"><div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div></td><td style="text-align: center;"><div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div></td></tr></tbody></table>				Predicted	Measured	C_{total}	<div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div>	<div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div>
	Predicted	Measured						
C_{total}	<div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div>	<div style="border: 1px solid black; width: 100px; height: 30px; display: inline-block;"></div>						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Analysis</div>								
Equation used to calculate C_{total} :								

file 01653

Answer 26

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 26

Many modern digital multimeters come equipped with capacitance measurement built-in. If your students do not have these meters, you will either need to provide one for them to use, or provide an LCR meter. If you don't have either one of these instruments, you should get one right away!

Competency: RC discharge circuit		Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 10px;"> <p style="text-align: center;">Pushbutton switch</p> <p style="text-align: center;">V_{supply} C_1 R_1 V Meter</p> </div>														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;">$V_{\text{supply}} =$</div> <div style="text-align: center;">$C_1 =$</div> <div style="text-align: center;">$R_1 =$</div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;">$t_1 =$</div> <div style="text-align: center;">$t_2 =$</div> <div style="text-align: center;">$t_3 =$</div> </div>														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 20%; text-align: center; border-bottom: 1px solid black;">Predicted</th> <th style="width: 20%; text-align: center; border-bottom: 1px solid black;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right; padding-right: 10px;">V_{t1}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t2}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t3}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </tbody> </table>				Predicted	Measured	V_{t1}			V_{t2}			V_{t3}		
	Predicted	Measured												
V_{t1}														
V_{t2}														
V_{t3}														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>														

Answer 27

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 27

I recommend choosing resistor and capacitor values that yield time constants in the range that may be accurately tracked with a stopwatch. I also recommend using resistor values significantly less than the voltmeter's input impedance, so that voltmeter loading does not significantly contribute to the decay rate.

Good time values to use (t_1 , t_2 , t_3) would be in the range of 5, 10, and 15 seconds, respectively.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Time-delay relay		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$C_1 =$	$R_{\text{coil}} =$	$V_{\text{dropout}} =$
Parameters			
t_{delay}	<div>Predicted <div style="border: 1px solid black; height: 20px; width: 100%;"></div></div>	<div>Measured <div style="border: 1px solid black; height: 20px; width: 100%;"></div></div>	
Calculations			

file 01647

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 28

Two very important "given" parameters are the relay coil resistance (R_{coil}) and the relay dropout voltage ($V_{dropout}$). These are best determined experimentally.

Many students fail to grasp the purpose of this exercise until it is explained. The idea here is to predict *when* the relay will "drop out" after the switch is opened. This means solving for t in the time-constant (decay) equation given the initial capacitor voltage, time constant (τ), and the capacitor voltage at time t . Because this involves the use of logarithms, students may be perplexed until given assistance.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: RC charge/discharge circuit		Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div style="text-align: center;">$V_{\text{supply}} =$</div> <div style="text-align: center;">$C_1 =$</div> <div style="text-align: center;">$R_1 =$</div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;">$t_1 =$</div> <div style="text-align: center;">$t_2 =$</div> <div style="text-align: center;">$t_3 =$</div> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; justify-content: space-between; margin-top: 20px;"> <div style="width: 45%;"> <p style="text-align: center; margin-bottom: 10px;"><i>Charging from 0 volts</i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right; padding-right: 10px;">V_{t1}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t2}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t3}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table> </div> <div style="width: 45%;"> <p style="text-align: center; margin-bottom: 10px;"><i>Discharging from V_{supply}</i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right; padding-right: 10px;">V_{t1}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t2}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{t3}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table> </div> </div>				Predicted	Measured	V_{t1}			V_{t2}			V_{t3}				Predicted	Measured	V_{t1}			V_{t2}			V_{t3}		
	Predicted	Measured																								
V_{t1}																										
V_{t2}																										
V_{t3}																										
	Predicted	Measured																								
V_{t1}																										
V_{t2}																										
V_{t3}																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>																										

file 01657

Answer 29

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 29

I recommend choosing resistor and capacitor values that yield time constants in the range that may be accurately tracked with a stopwatch. I also recommend using resistor values significantly less than the voltmeter's input impedance, so that voltmeter loading does not significantly contribute to the decay rate.

Good time values to use (t_1 , t_2 , t_3) would be in the range of 5, 10, and 15 seconds, respectively.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Rate of change indicator circuit		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_{\text{pot}} =$	$C_1 =$	$R_1 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
<i>Qualitative answers only</i>			
	Predicted	Measured	
V_{out} Wiper up, slowly	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	
V_{out} Wiper down, slowly	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	
V_{out} Wiper up, rapidly	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	
V_{out} Wiper down, rapidly	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Analysis</div>			
Explain <i>why</i> the output voltage polarity is related to the wiper motion as measured.			

file 03178

Answer 30

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 30

I recommend a supply voltage of 12 volts, a potentiometer value of 10 k Ω , a capacitor value of 0.1 μ F, and a loading resistor (R_1) of 1 M Ω . Use a DMM so as to not load the circuit any more than necessary. If you wish to choose different capacitor/resistor values, I strongly suggest choosing them such that the time constant (τ) of the circuit significantly faster than 1 second.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

(Template)

Competency:	Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>							
<table style="margin-left: auto; margin-right: auto;"><tr><td style="text-align: center; padding: 5px;">Predicted</td><td style="text-align: center; padding: 5px;">Measured</td></tr><tr><td style="text-align: center; padding: 5px;"><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td><td style="text-align: center; padding: 5px;"><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td></tr><tr><td style="text-align: center; padding: 5px;"><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td><td style="text-align: center; padding: 5px;"><div style="border: 1px solid black; width: 80px; height: 25px;"></div></td></tr></table>		Predicted	Measured	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>
Predicted	Measured						
<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>						
<div style="border: 1px solid black; width: 80px; height: 25px;"></div>	<div style="border: 1px solid black; width: 80px; height: 25px;"></div>						

file 01602

Answer 31

Here, you would indicate where or how to obtain answers for the requested parameters, but not actually give the figures. My stock answer here is “use circuit simulation software” (Spice, Multisim, etc.).

Notes 31

Any relevant notes for the assessment activity go here.