

Resistance, Reactance, and Impedance worksheet

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

This worksheet covers the following concepts:


- Phase relations of voltage and current in an inductive AC circuit. (PENDING).
- Phase relations of voltage and current in a capacitive AC circuit. (PENDING).
- Calculation of inductive reactance (PENDING).
- Calculation of capacitive reactance (PENDING).
- Combinations of reactance and resistance (PENDING).
- Vectors and trigonometry review (PENDING).

Resources and methods for learning about these subjects (list a few here, in preparation for your research):

Questions

Question 1

What will happen to the brightness of the light bulb as the iron core is moved away from the wire coil in this circuit? Explain why this happens.

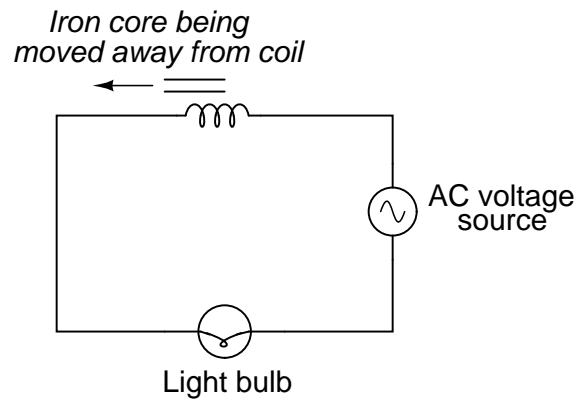

file 00095

Answer 1

The light bulb will glow brighter when the iron core is moved away from the wire coil, due to the change in inductive reactance (X_L).

Notes 1

One direction you might want to lead your students in with this question is how AC power may be controlled using this principle. Controlling AC power with a variable *reactance* has a definite advantage over controlling AC power with a variable *resistance*: less wasted energy in the form of heat.